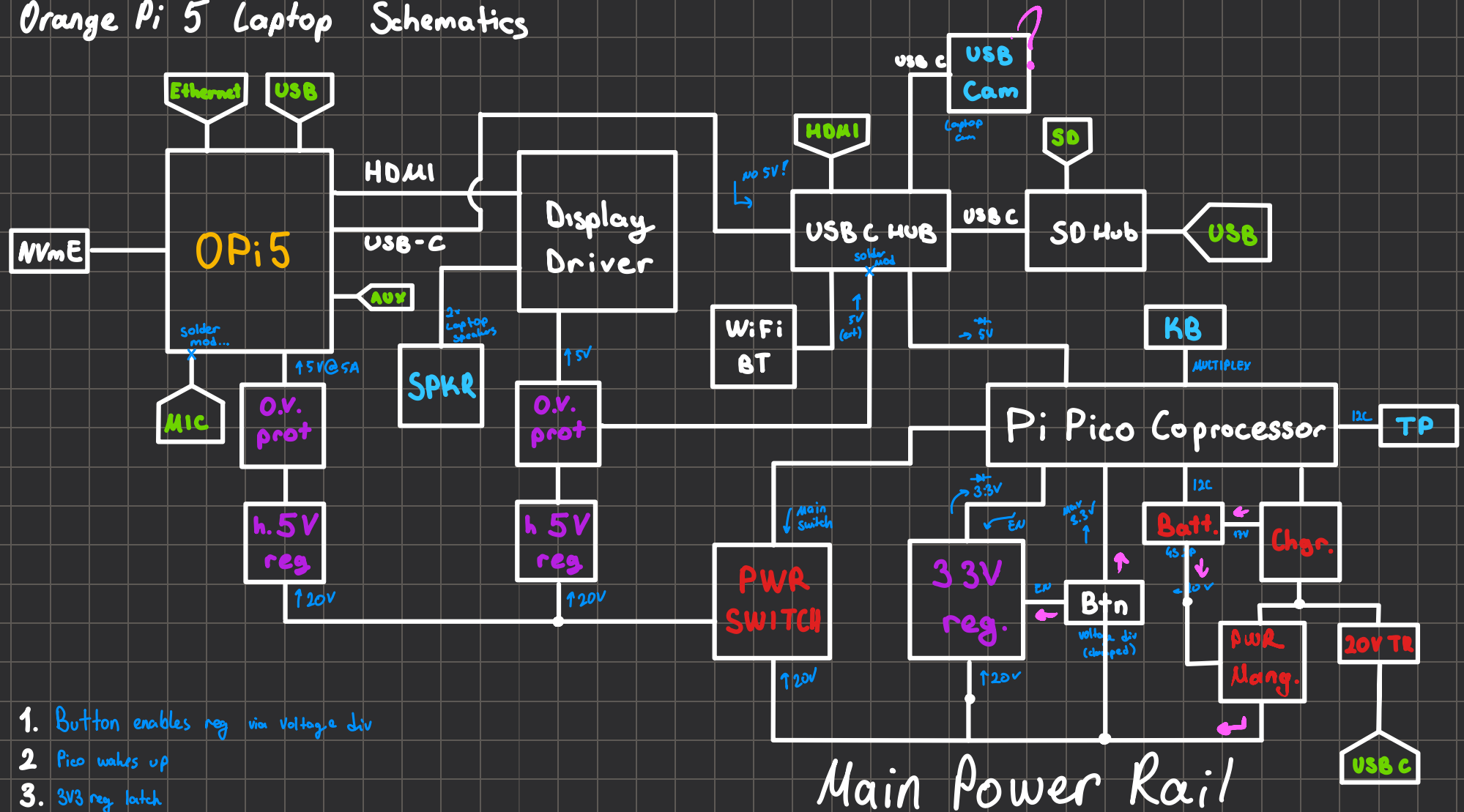


Orange Pi 5 Laptop Schematics



1. Button enables reg via voltage div
2. Pico wakes up
3. 3V3 reg. latch
4. Main power on